

**NAMIBIA UNIVERSITY  
OF SCIENCE AND TECHNOLOGY**

**FACULTY OF HEALTH AND APPLIED SCIENCES**

**DEPARTMENT OF NATURAL AND APPLIED SCIENCES**

<b>QUALIFICATION:</b> BACHELOR OF SCIENCE (MAJOR AND MINOR)	
<b>QUALIFICATION CODE:</b> 07BOSC	<b>LEVEL:</b> 6
<b>COURSE NAME:</b> ELECTRICAL CIRCUIT AND ELECTRONICS	<b>COURSE CODE:</b> ECE602S
<b>SESSION:</b> JANUARY 2020	<b>PAPER:</b> THEORY
<b>DURATION:</b> 3 HOURS	<b>MARKS:</b> 100

<b>SUPPLEMENTARY/SECOND OPPORTUNITY EXAMINATION QUESTION PAPER</b>	
<b>EXAMINER (S)</b>	EMMANUEL EJEMBI
<b>MODERATOR:</b>	SAHU DIPTI

**PERMISSIBLE MATERIALS**

Scientific Calculator

**THIS EXAMINATION QUESTION PAPER CONSISTS OF 7 PAGES**

**(INCLUDING THIS FRONT PAGE)**

## SECTION A

### QUESTION 1

[30]

Short Answer Question Types: Each question in this section carries two marks.

1.1 To obtain p-type semiconductor, the impurity added to a pure semiconductor is (2)

- a. Trivalent      b. Tetravalent      c. Pentavalent      d. None of these

1.2 A p-type and n-type semiconductor attend positive and negative charge respectively. (2)

- a. True      b False

1.3 In an N-type semiconductor the majority carriers are (2)

- a. Holes      b. Electrons      c. Positive ions      d. Negative ions

1.4 For Germanium PN Junction the maximum value of barrier potential is (2)

- a. 0.3 volt      b. 0.1 volt      c. 1.3 volt      d. 1.7 volt

1.5 When a PN Junction is reverse biased. (2)

- a. The beat of the depletion layer increases  
b. It offers the high resistance  
c. A small current flows through it because of minority carriers  
d. All of these

1.6 In a half wave rectifier, the load current flows (2)

- a. Only for the positive of cycle of the input signal  
b. For less than half cycle of the input signal  
c. For more than half cycle of the input signal  
d. For whole cycle of the input signal

1.7 Zener diode is used as (2)

- a. An amplifier      b. A voltage regulator      c. A coupler      d. A rectifier

- 1.8 In an npn transistor with normal bias (2)
- a. Only holes cross the collector junction
  - b. Only the majority carriers cross the collection junction
  - c. The emitter junction has a high resistance
  - d. The emitter junction is forward biased and collector junction is reverse biased
- 1.9 A transistor is said to be in quiescent state when (2)
- a. It is unbiased
  - b. No Current flows through it
  - c. Emitter junction is just biased equal to collector junction.
  - d. No signal is applied to the input
- 1.10 In a pnp transistor, the current carriers are (2)
- A Acceptor ions   b. Donor ions   c. Free electrons   d. Holes
- 1.11 Most of the majority carriers from the emitter (2)
- a. Recombine in the base
  - b. Recombine in the emitter
  - c. Pass through the base region to the collector
  - d. None of these.
- 1.12 When transistor are used in digital circuits, they usually operate in the (2)
- a. Active region   b. Breakdown region   c. Saturated and cutoff region
  - d. Linear region
- 1.13 In a transistor, Collector current is controlled by (2)
- a. Collector voltage   b. Base current\_   c. Collector resistor
  - d. All of the above

1.14 Which of the following load line equation is correct? (2)

a.  $V_{CC} = V_{CE} - I_C R_L$     b.  $V_{CE} = V_{CC} - I_C R_L$     c.  $I_C R_L = V_{CC} - V_{CE}$

d.  $V_{CE} = V_{CC} + I_C R_L$

1.15 A differential amplifier has an open-loop voltage gain of 120. The input signals are (2)

2.45V and 2.35V. Calculate the output voltage of the amplifier

- a. 12V    b. 14V    c. 13V    d. 9V

**SECTION B**

**QUESTION 2**


[15]

2.1 Define Kirchhoff's Current Law.

(2)

2.2 For the networks shown in **figure 2.1** below, find the values of the currents marked.


(5)

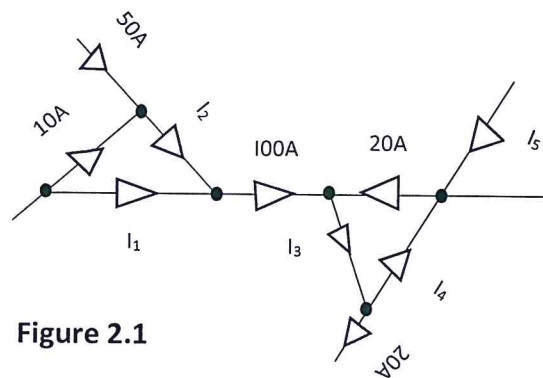

**Figure 2.1**

2.3 Determine the value of e.m.f.  $E$  in the circuit shown in **figure 2.2** below

(8)

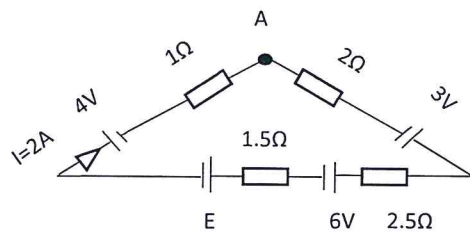

**Figure 2.2**

**QUESTION 3**

[15]

3.1 State Thevenin's Theorem.


(2)

3.2 List the procedure adopted when using Thevenin's Theorem to find current in an Electric circuit.

(4)

3.3 Use Thevenin's theorem to find the current flowing in the  $14 \Omega$  resistor of the network shown in **Figure 3.1**.

(6)

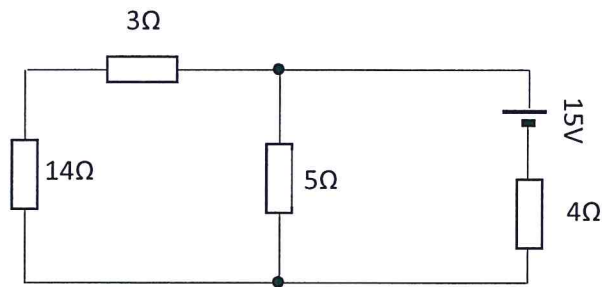

**Figure 3.1**

3.4 Use the calculated current in **question 3.3** and find also the power dissipated in the 14 Ω Resistor of **Figure 3.1** above. (3)

**QUESTION 4** [15]

4.1 What do you understand by forward biased in semiconductor? (2)

4.2 Sketch the reverse characteristics of a germanium and silicon p-n junction diode and describe the shapes of the characteristics. (5)

4.3 Explain full wave rectifier diode. (3)

4.4 Draw a full-wave rectifier circuit and explain what happened to the diode during positive and negative cycle of the input. (5)

**QUESTION 5** [15]

5.1 Define Transistor. (2)

5.2 Briefly explain the following region of operation of a bipolar junction transistor (BJT). (2)

- i. Active region.
- ii. Operating point (Q-point).

5.3 State the full meaning of the following abbreviation in a bipolar junction transistor (BJT) circuit.  $V_{EB}$ ,  $V_{CB}$ ,  $V_{EE}$ ,  $V_{CC}$  and  $V_{CE}$ . (5)

5.4 A transistor amplifier, supplied from a 9V battery, require a DC bias current of  $100\mu\text{A}$ . (6)  
What value of bias resistor would be connected from base to the  $V_{CC}$  line if

- i.  $V_{CE}$  is ignored
- ii.  $V_{CE}$  is 0.6V.

### QUESTION 6

[10]

6.1 Briefly explain the following operational amplifier parameters. (3)

- i. The input bias current ( $I_B$ )
- ii. Input offset current ( $I_{os}$ )
- iii. Input offset voltage.

6.2 Draw an operational amplifier voltage characteristic showing how the out  $V_o$  varies (3)  
with the input ( $V_2 - V_1$ ).

6.3 Determine the common-mode gain of an op amp that has a differential voltage gain of (4)  
 $150 \times 10^3$  and a Common mode rejection of 90 dB.