



**NAMIBIA UNIVERSITY  
OF SCIENCE AND TECHNOLOGY**

**FACULTY OF HEALTH AND APPLIED SCIENCES**

**DEPARTMENT OF NATURAL AND APPLIED SCIENCES**

<b>QUALIFICATION : BACHELOR OF SCIENCE</b>	
<b>QUALIFICATION CODE: 07BOSC</b>	<b>LEVEL: 7</b>
<b>COURSE CODE: ECE602S</b>	<b>COURSE: ELECTRICAL CIRCUITS &amp; ELECTRONICS</b>
<b>SESSION: JANUARY 2019</b>	<b>PAPER: THEORY</b>
<b>DURATION: 3 Hours</b>	<b>MARKS: 100</b>

<b>SECOND OPPORTUNITY/SUPPLEMENTARY EXAMINATION PAPER</b>	
<b>EXAMINER</b>	Dr Munawar Karim
<b>MODERATOR:</b>	Mr. Vaino Indongo

<p style="text-align: center;"><b>INSTRUCTIONS</b></p> <ol style="list-style-type: none"><li>1. Write all your answers in the answer booklet provided</li><li>2. Read the whole question before answering</li><li>3. Begin each question on a new page.</li></ol>
-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

**PERMISSIBLE MATERIALS**

Non-programmable scientific calculator

**ATTACHMENTS**


None

**THIS PAPER CONSISTS OF 4 PAGES**

(Including this front page)

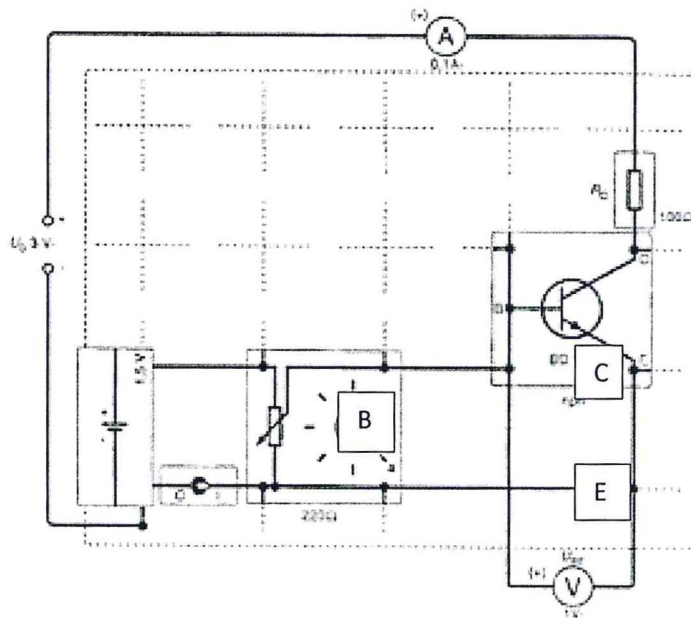
- 1) A band-pass filter passes a range of frequencies while blocking signals on either side of the band. Design a low-pass circuit with the 3dB point at 500Hz. Provide a circuit diagram and component values (choose values of R and C). (15)
- 2) Calculate  $v_o/v_i$  as a function of R, C and frequency  $f$ . Draw a graph of  $20\log v_{out}/v_{in}$  vs  $\log f$ . Identify the 3dB point. (15)
- 3) Design a high-pass circuit with the 3dB point at 1000Hz. Provide a circuit diagram and. (15)  
component values (choose values of R and C).
- 4) Calculate  $v_o/v_i$  as a function of R, C and frequency  $f$ . Draw a graph of  $20\log v_{out}/v_{in}$  vs  $\log f$ . Identify the 3dB point. (15)
- 5) Draw a circuit of a low- and high-pass filters to make a band-pass filter. (15)
- 6) A transistor circuit is shown below. (15)

The potentiometer is adjusted for different resistances.



- (i) In the table below are recorded measured values of the base voltage  $U_{BE}$  and collector current  $I_C$ . Plot the value pairs  $U_{BE}$  and  $I_C$  in the graph.


Step ►	4	10	11	14
Base-emitter voltage $\frac{U_{BE}}{V}$	Collector current $\frac{I_C}{mA}$	Voltage drop at resistor $R$ $\frac{U_R}{V}$	Collector-emitter voltage $\frac{U_{CE}}{V}$	Collector-emitter resistance $R_{CE} = \frac{U_{CE}}{I_{CE}}$ ( $\Omega$ )
0	0	0	3.0	$\infty$
0.1	0	0	3.0	$\infty$
0.2	0	0	3.0	$\infty$
0.3	0	0	3.0	$\infty$
0.4	0	0	3.0	$\infty$
0.45	0	0	3.0	$\infty$
0.50	0	0	3.0	$\infty$
0.55	0	0	3.0	$\infty$
0.60 x	1.0	0.1	2.9	2900
0.65	6.0	0.6	2.4	400
0.70	20	2.0	1.0	50
0.75 x	30	3.0	0	0
0.80	30	3.0	0	0

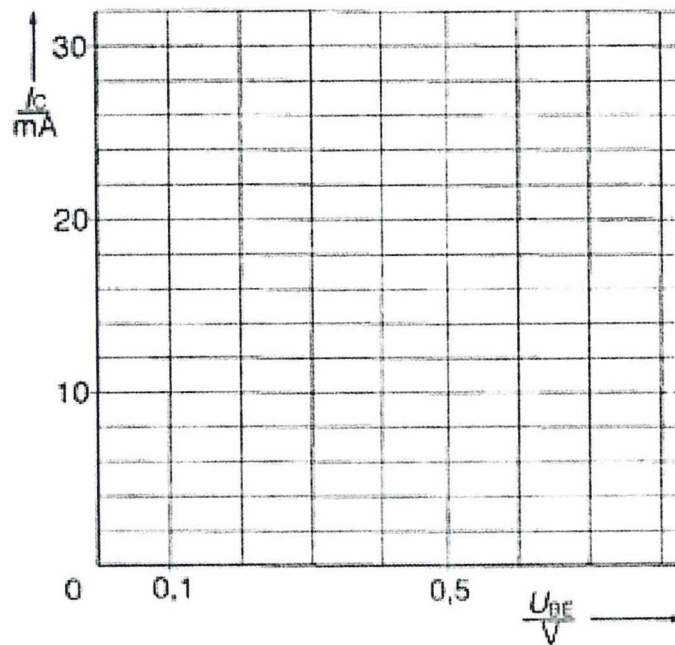

- (ii) At what voltage  $U_{BE1}$  does the collector-emitter path of the transistor become conductive?

- (iii) At what value  $U_{BE2}$  does the collector current  $I_c$  stop changing?
- (iv) Why does  $I_c$  not increase any further? Hint: there is a  $100\Omega$  resistor in series with the collector.

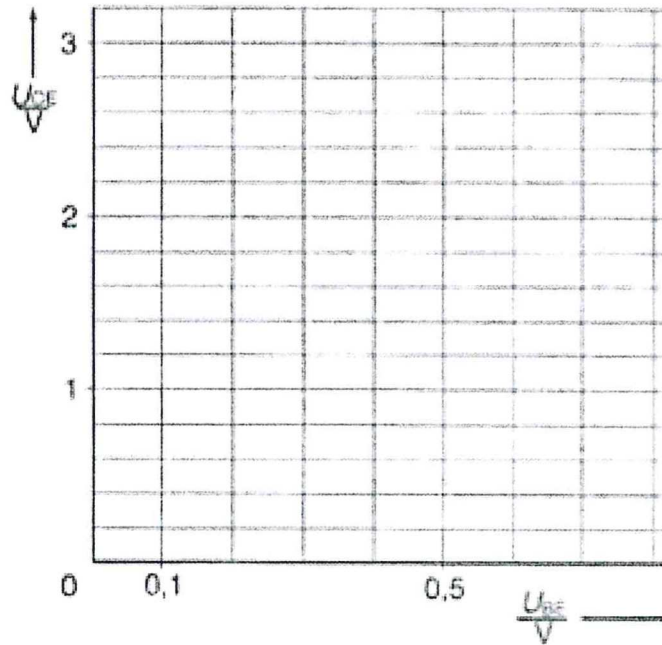(7) (i) Draw the graph for  $U_{CE}$  as a function of  $U_{BE}$  in the graph below, using information on the table above. (10)



- (ii) Calculate the slope of the characteristic in the middle between  $U_{BE1}$  and  $U_{BE2}$ . This is the working voltage of the transistor.
- (iii) For which base-emitter voltages is the transistor an insulator, and for which voltages is it a conductor?