



NAMIBIA UNIVERSITY
OF SCIENCE AND TECHNOLOGY

**Faculty of Health, Natural
Resources and Applied
Sciences**

School of Natural and Applied
Sciences

Department of Biology,
Chemistry and Physics

13 Jackson Kaujeua Street T: +264 61 207 2012
Private Bag 13388 F: +264 61 207 9012
Windhoek E: dbcp@nust.na
NAMIBIA W: www.nust.na

QUALIFICATION : BACHELOR OF SCIENCE	
QUALIFICATION CODE: 07BOSC	LEVEL: 6
COURSE: ELECTRICAL CIRCUITS AND ELECTRONICS	COURSE CODE: ECE602S
DATE: JANUARY 2024	SESSION: 1
DURATION: 3 HOURS	MARKS: 100

SECOND OPPORTUNITY / SUPPLEMENTARY: EXAMINATION QUESTION PAPER

EXAMINER: PROF MUNAWAR KARIM

MODERATOR: DR VAINO INDONGO

INSTRUCTIONS

1. Answer all questions on the separate answer sheet.
2. Please write neatly and legibly.
3. Do not use the left side margin of the exam paper. This must be allowed for the examiner.
4. No books, notes and other additional aids are allowed.
5. Mark all answers clearly with their respective question numbers.

PERMISSIBLE MATERIALS:

1. Non-Programmable Calculator

This paper consists of 2 pages including this front page

- 1) Describe an experiment to measure the open circuit voltage of a cell. Show the circuit components needed as well as meters required for the measurement. (40)
- 2) Draw a circuit diagram for an inverting amplifier with a gain of ten. Label all components. (20)
- 3) For a sinusoidal signal the current output of a circuit lags 90° behind the input. Identify the circuit component. Provide your reasoning. (20)
- 4) For a sinusoidal signal the voltage output of a circuit leads the input by 90° . Identify the circuit component. Provide your reasoning. (10)
- 5) A sinusoidal signal needs to be attenuated by a factor of 1000 at a frequency of 1000 Hz. Design a circuit that will meet the requirements. Calculate and identify the components. (10)

END OF QUESTION PAPER